

MULTI-CYCLE PROCESSOR

Lecturer: Hui Annie Guo


h.guo@unsw.edu.au

K17-501F

Lecture overview

- **Topics**
 - **Motivation**
 - **Multi-cycle processor**
 - **Datapath**
 - **Control**
- **Suggested reading**
 - **H&P B.11**
 - **Reference**
 - **H&P textbook (3rd edition) on MC processor**
 - Page 318-340


Recall: Single cycle processor

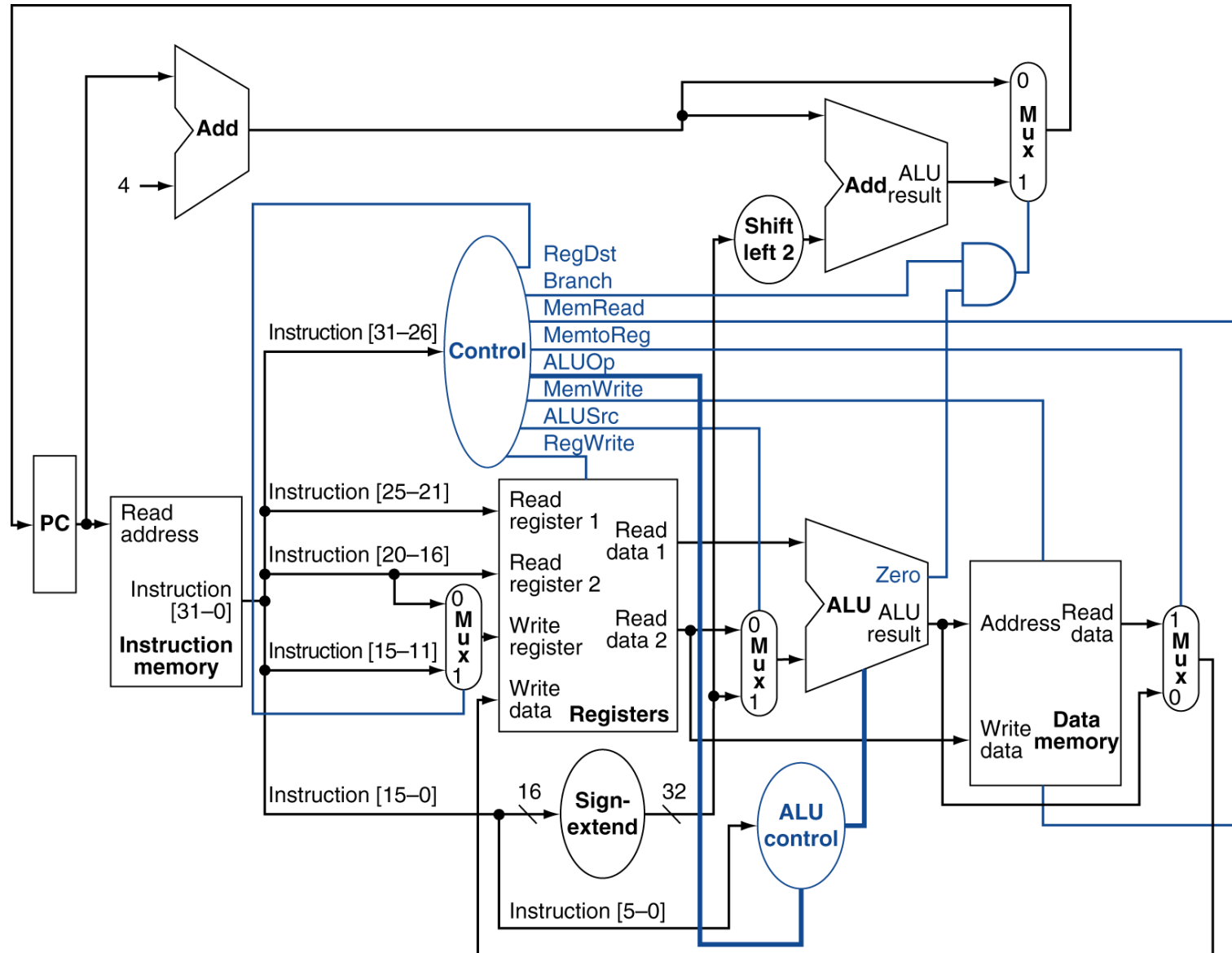

Latency of ADDU and SUBU

PC	IM	RF	MUX	ALU	MUX	setup
----	----	----	-----	-----	-----	-------

 
Assume control signals are ready when data flow to a component



Latency of ORI

PC	IM	RF	MUX	ALU	MUX	setup
----	----	----	-----	-----	-----	-------

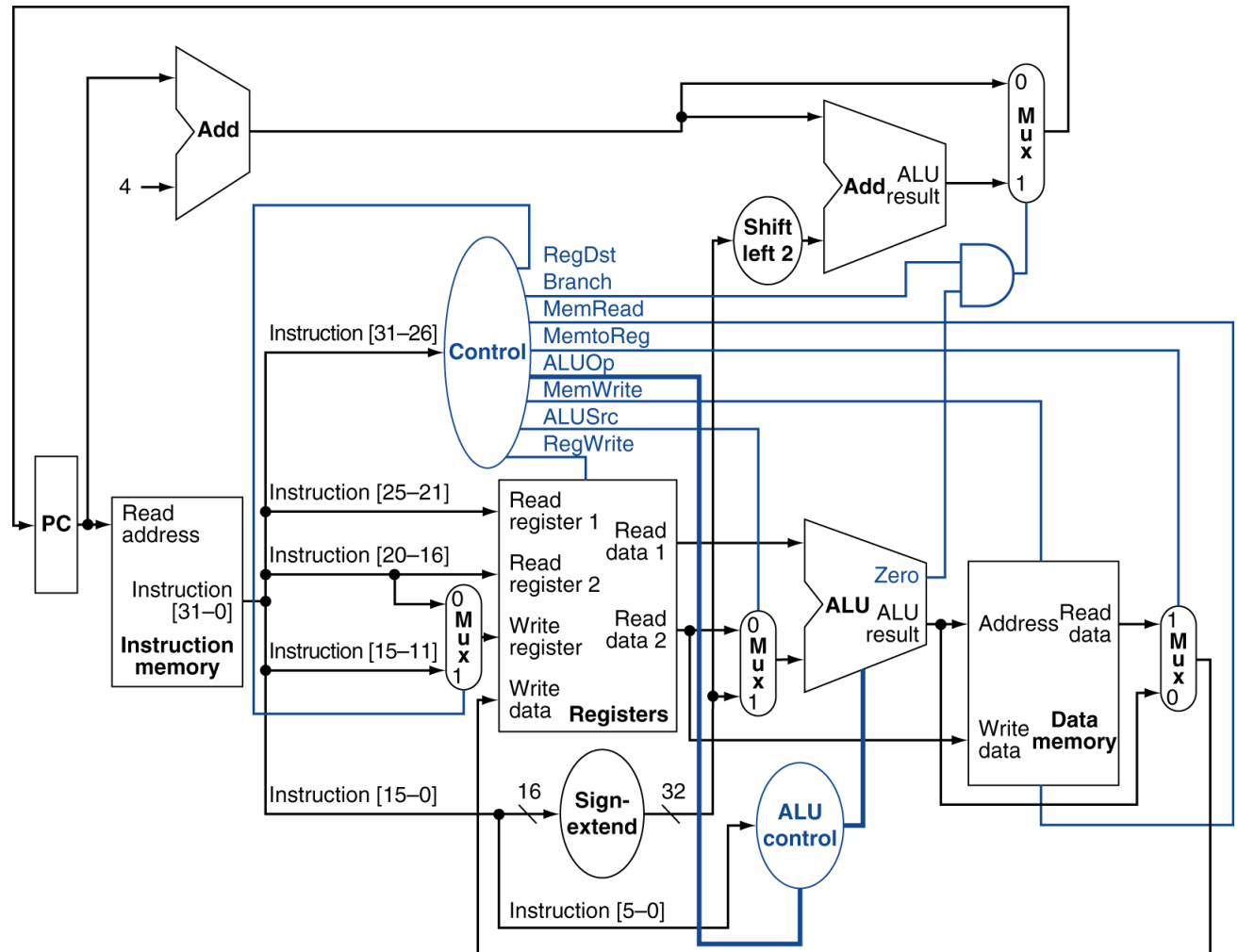
Assume control signals are ready when data flow to a component



Latency of LW

PC	IM	RF	MUX	ALU	DM	MUX	setup
----	----	----	-----	-----	----	-----	-------

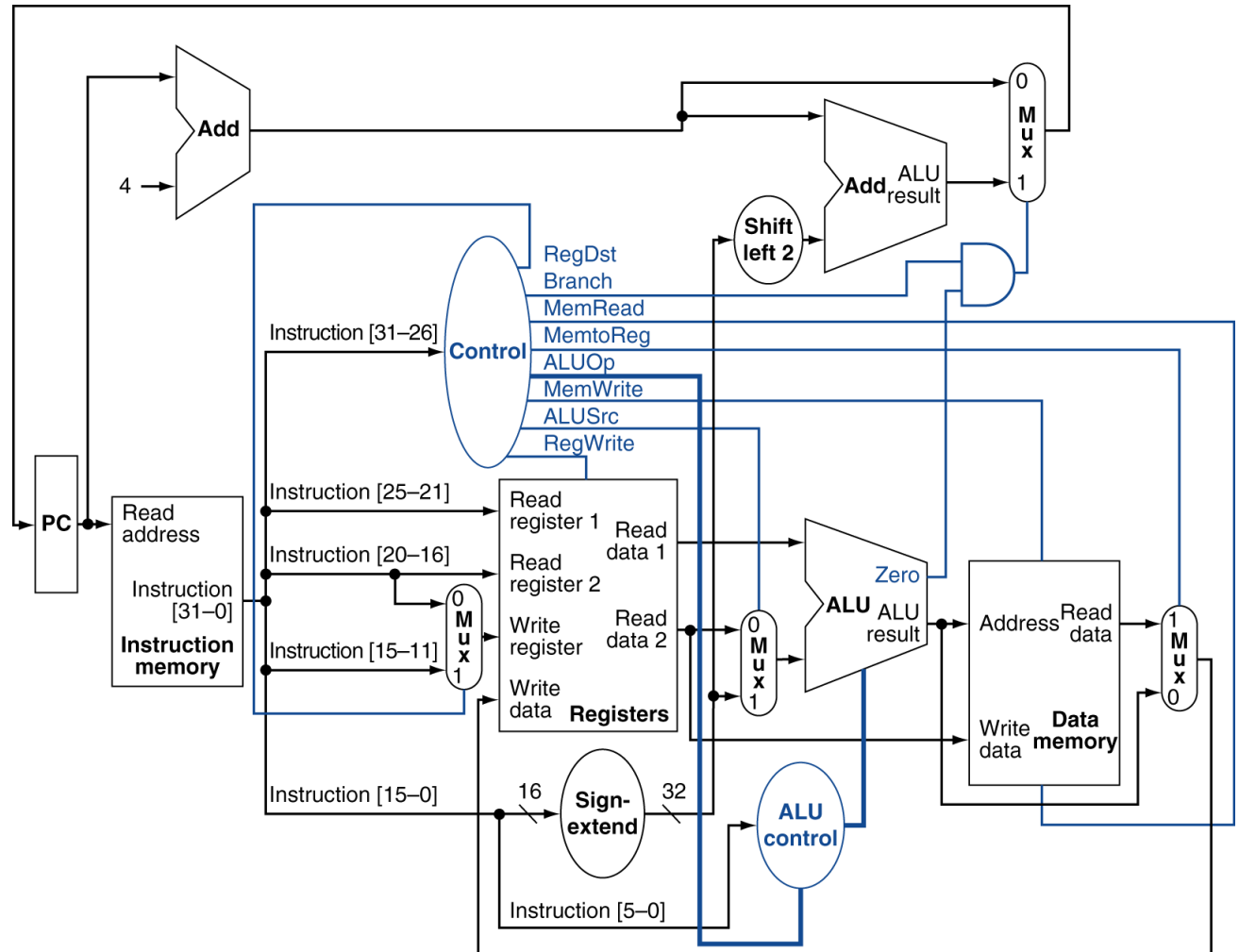
Assume control signals are ready when data flow to a component



Latency of SW

PC	IM	RF	MUX	ALU	DM	MUX	setup
----	----	----	-----	-----	----	-----	-------

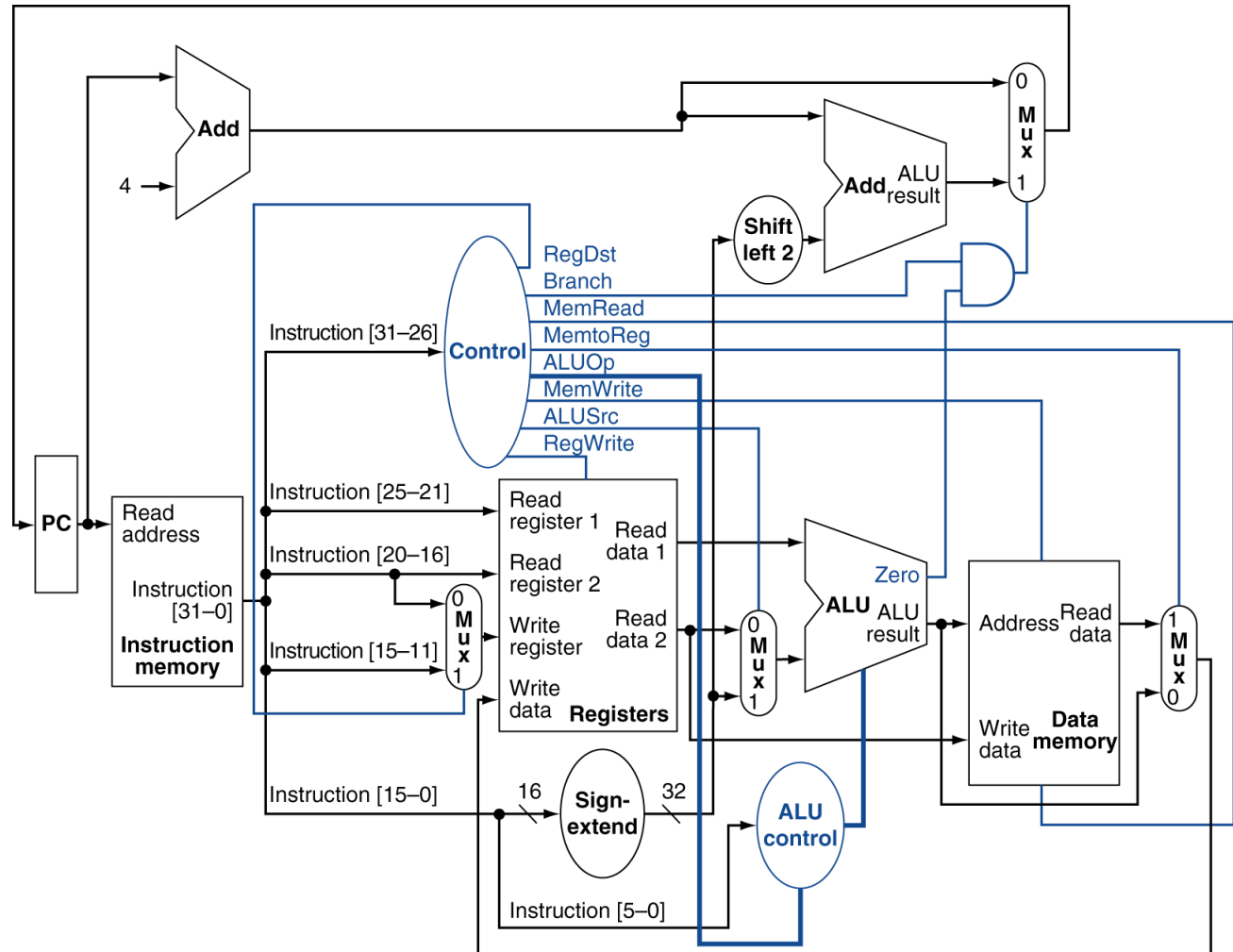
Assume control signals are ready when data flow to a component



Latency of BEQ


PC	IM	RF	MUX	ALU	setup
----	----	----	-----	-----	-------

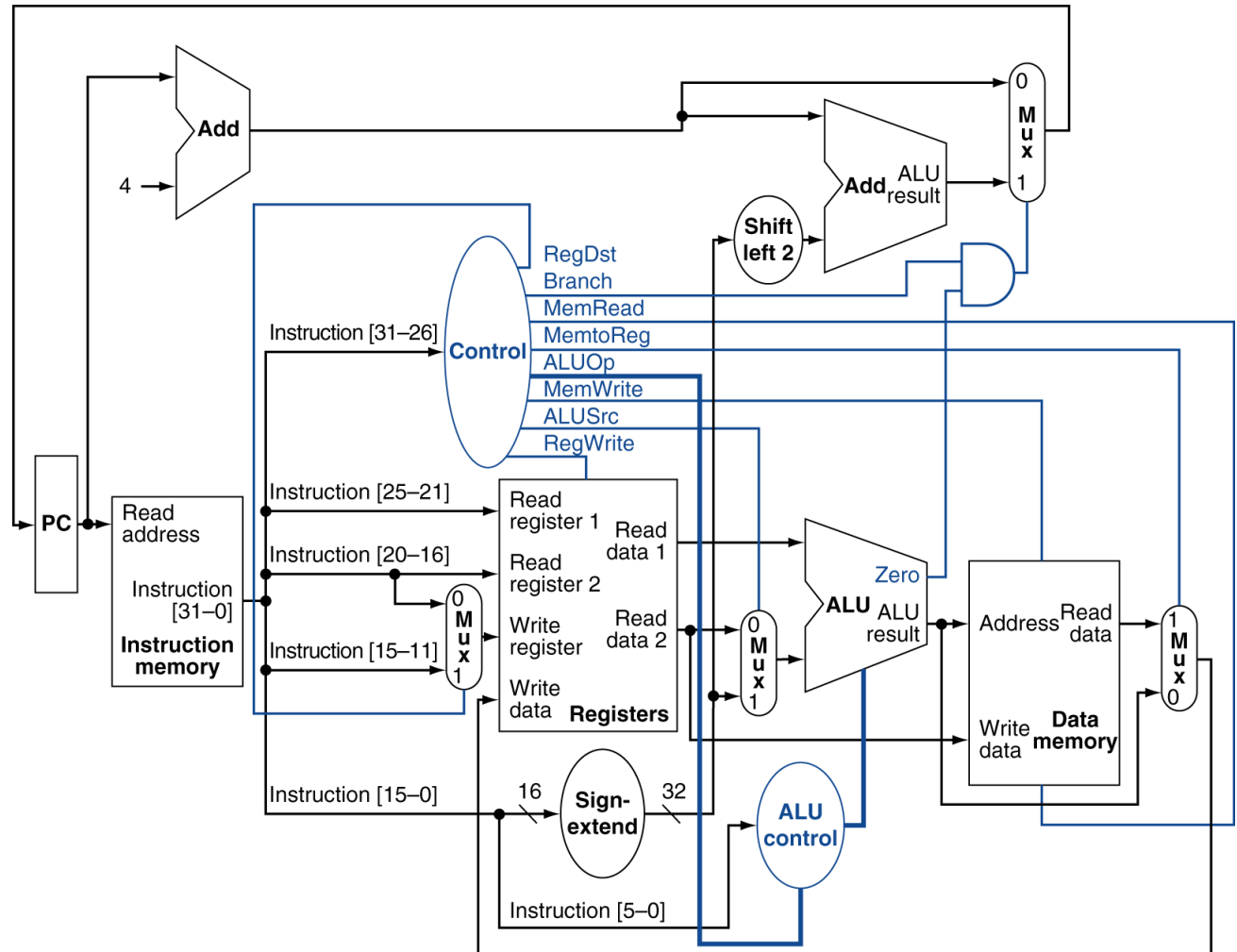Assume control signals are ready when data flow to a component




Multi-cycle datapath

 - **With reduced clock cycle time**
- **An instruction is completed in multiple clock cycles**
 - each instruction uses as a small number of clock cycles as possible



How to implement multi-cycle processor?

 - **Partition the single-cycle datapath**
 - Try to balance time spent in each section
 - The clock cycle time is determined by the longest section delay
- **Insert registers between sections**
 - Based on the operation of each section




Note: Data flow backwards not presented

Operations of each section

- **Next address logic**
 $PC \leftarrow \text{branch ? } PC + 4 + \text{offset} : PC + 4$
- **Instruction fetch**
 $IR \leftarrow \text{Mem}[PC]$
- **Operand fetch**
 $A \leftarrow R[\text{rs}]$
 $B \leftarrow R[\text{rt}]$
- **ALU exec**
 $S \leftarrow A \text{ op } B$

- **Memory read**
 $M \leftarrow \text{Mem}[\text{Addr}]$
- **Memory write**
 $\text{Mem}[\text{addr}] \leftarrow B$
- **Write back**
 $R[\text{rd|rt}] \leftarrow R|M$

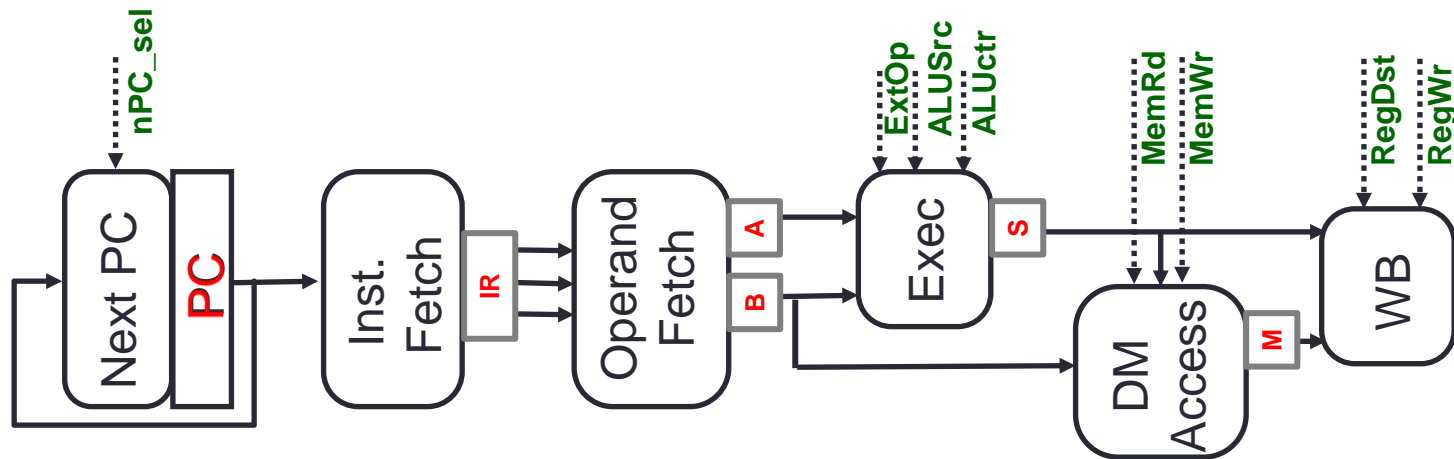

Operations of R-type instructions


Can be done in 4 clocks:

1 st clock:	$IR \leftarrow IM[PC]$
2 nd clock:	$A \leftarrow R[rs]; B \leftarrow R[rt]$
3 rd clock:	$S \leftarrow A \text{ op } B$
4 th clock:	$R[rd] \leftarrow S; PC \leftarrow PC+4$

 Example:

ADDU \$1, \$2, \$3

$\$1 \leftarrow \$2 + \$3, PC \leftarrow PC+4$



Operations of I-type logic instructions


Can be done in 4 clocks:

Example:

`Ori $1, $2, imm`

$\$1 \leftarrow \$2 \text{ or Zero_ext}(imm), PC \leftarrow PC+4$

1 st clock:	$IR \leftarrow IM[PC]$
2 nd clock:	$A \leftarrow R[rs]$
3 rd clock:	$S \leftarrow A \text{ or Zero_ext}(imm)$
4 th clock:	$R[rt] \leftarrow S; PC \leftarrow PC+4$

 

Operations of LW instruction


Can be done in 5 clocks:

1st clock: $IR \leftarrow IM[PC]$
 2nd clock: $A \leftarrow R[rs]; B \leftarrow R[rt]$
 3rd clock: $S \leftarrow A + \text{Sign_ext}(imm)$
 4th clock: $M \leftarrow DM[S]$
 5th clock: $R[rt] \leftarrow S; PC \leftarrow PC+4$

 Example:

LW \$1, \$2, imm

$\$1 \leftarrow DM[\$2 + \text{Sign_ext}(imm)], PC \leftarrow PC+4$



Operations of SW instruction


Can be done in 4 clocks:

Example:

SW \$1, \$2, imm

$DM[\$2 + \text{Sign_ext}(\text{imm})] \leftarrow \$1, PC \leftarrow PC + 4$

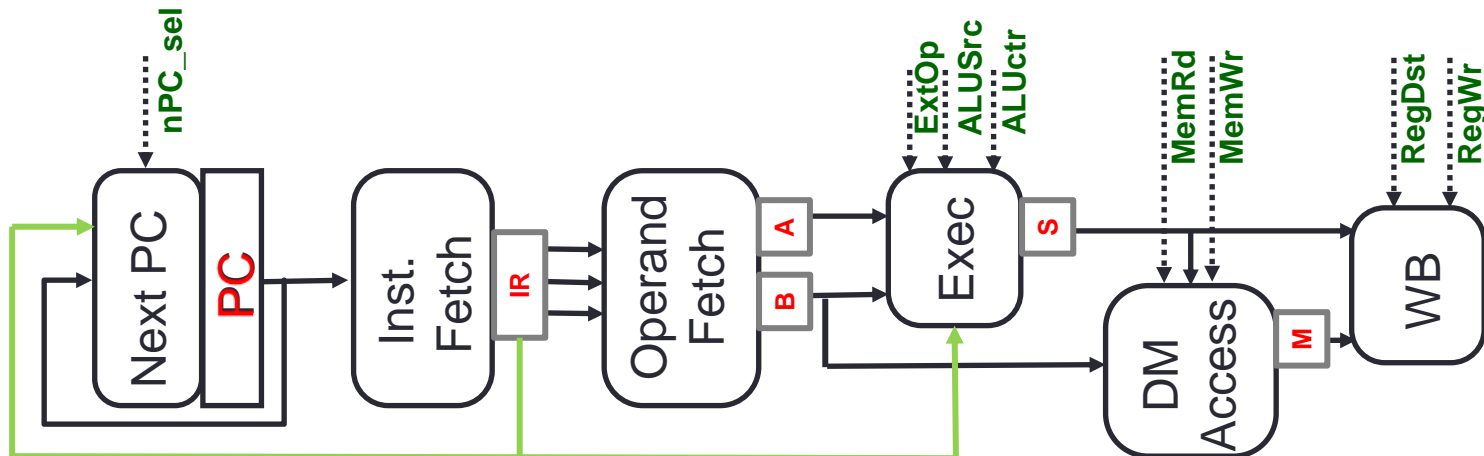1st clock: $IR \leftarrow IM[PC]$
 2nd clock: $A \leftarrow R[rs], B \leftarrow R[rt]$
 3rd clock: $S \leftarrow A + \text{Sign_ext}(\text{imm})$
 4th clock: $DM[S] \leftarrow B$



Operations of BEQ instruction


Can be done in 4 clocks:

Example:


BEQ \$1, \$2, imm

$\$1 == \$2, PC \leftarrow PC+4: PC+4+Sign_ext(imm)||00$


1 st clock:	$IR \leftarrow IM[PC]$
2 nd clock:	$A \leftarrow R[rs], B \leftarrow R[rt]$
3 rd clock:	$S \leftarrow A - B$
4 th clock:	$PC \leftarrow (PC+4 \text{ or } PC+4+Sign_ext(imm) 00)$

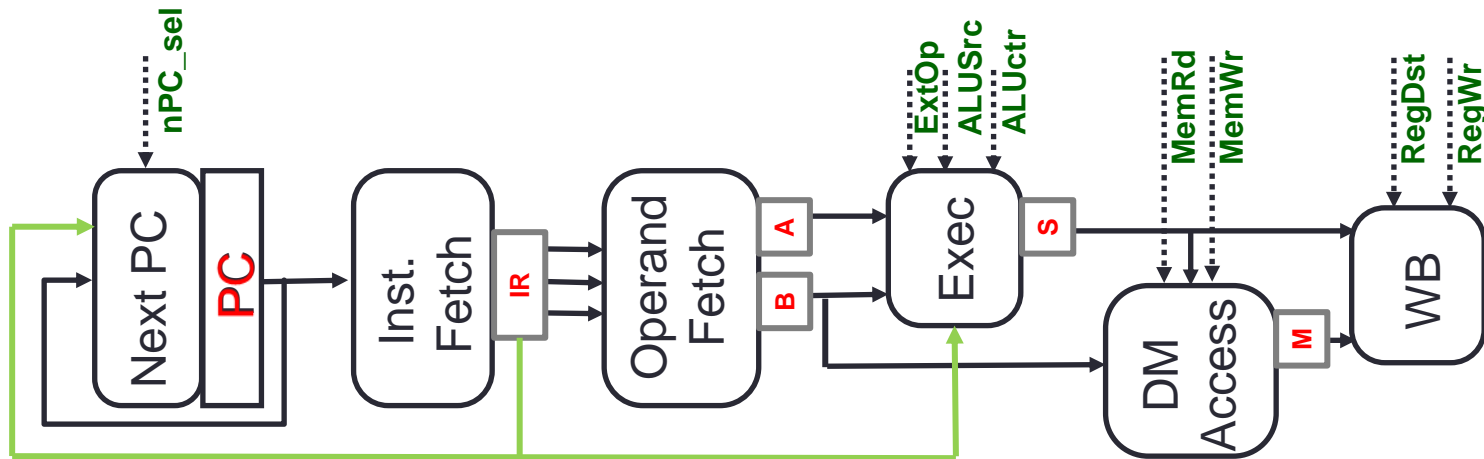

FSM for control

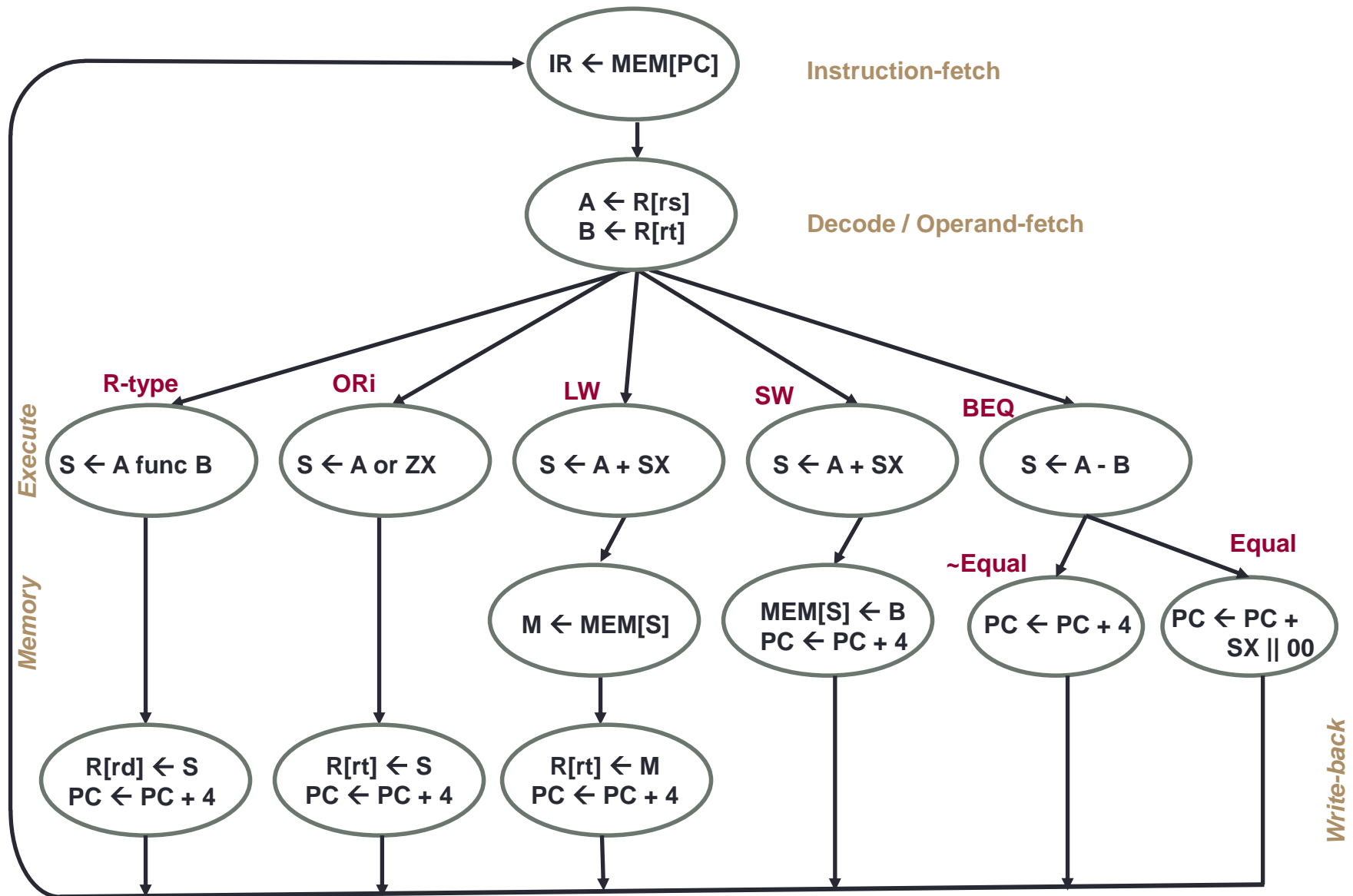

Example of multi-cycle processor

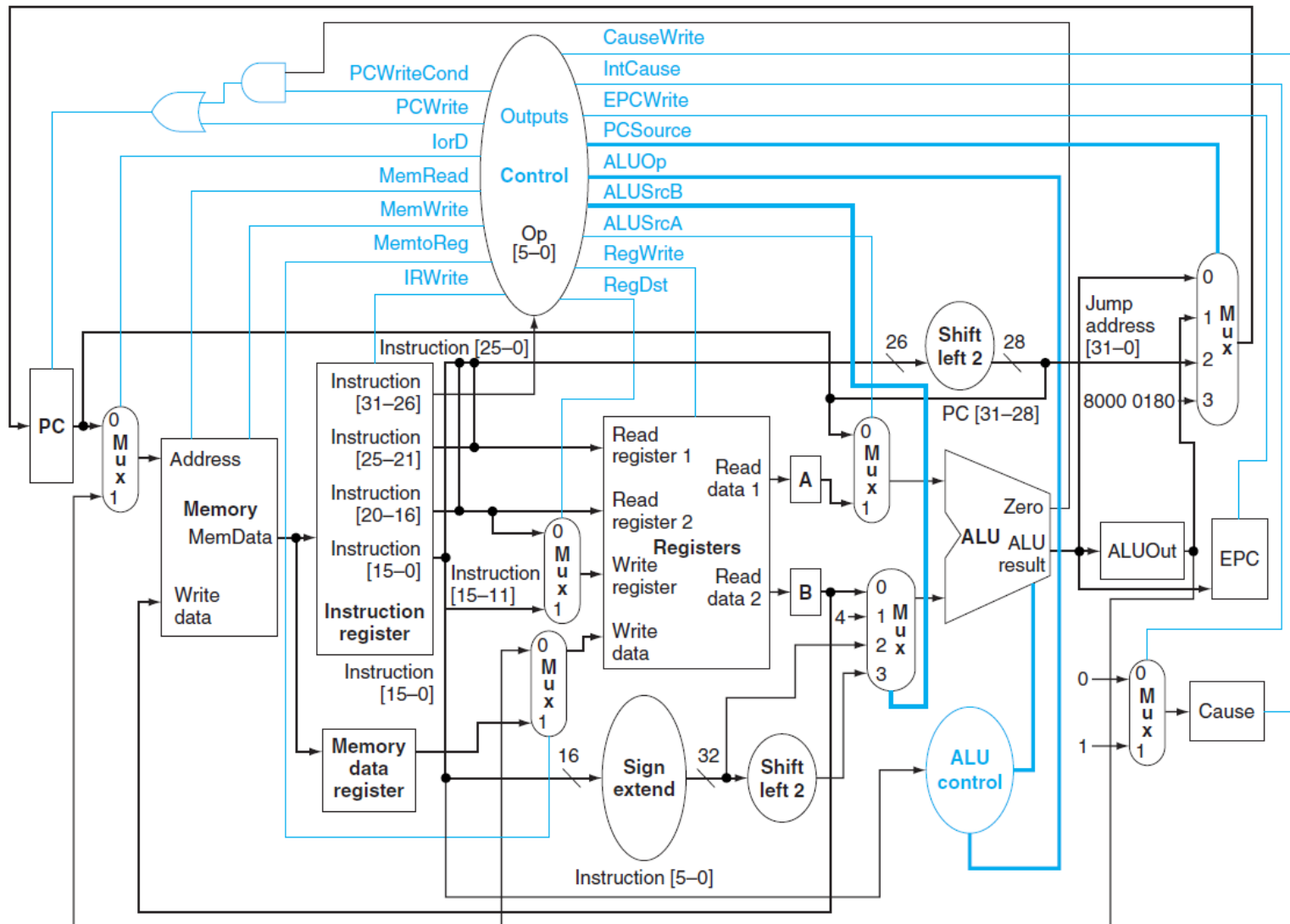


In-class exercise (1)

- Investigate how resource sharing is applied in the multi-cycle processor design shown in the previous slide.


In-class exercise (2)

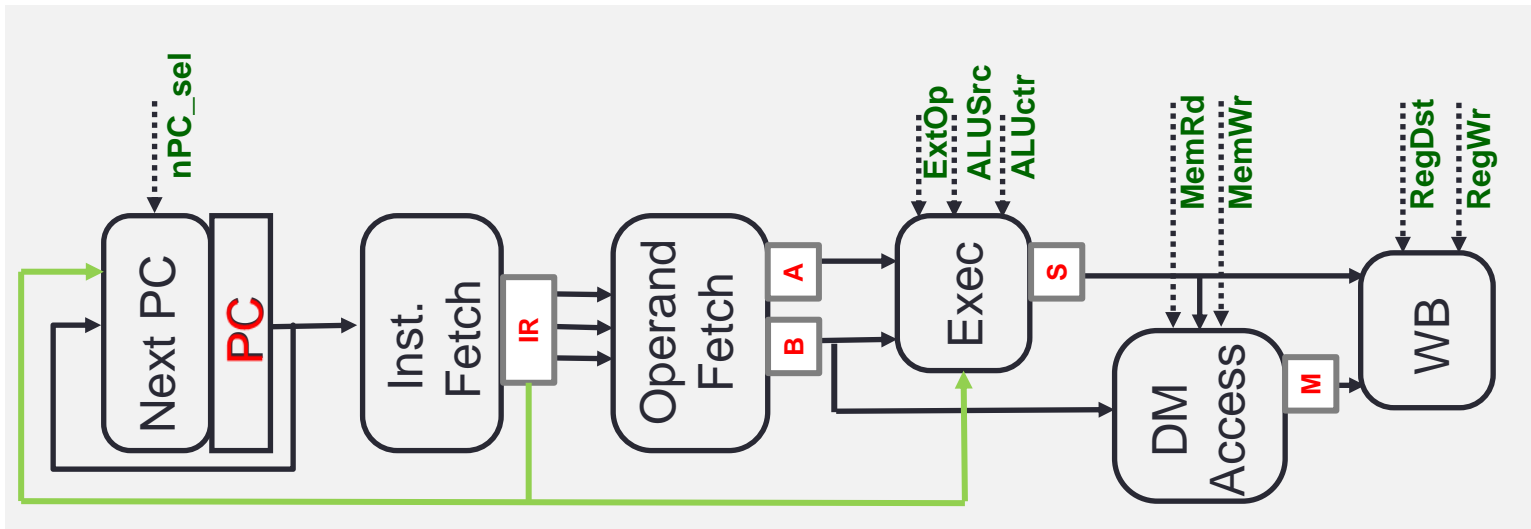- Based on the logic structure of the multi-cycle processor we discussed (as shown below), identify the datapath components in the example MC processor for the following operations:
 - (a) instruction fetch
 - (b) memory access




In-class exercise (3)

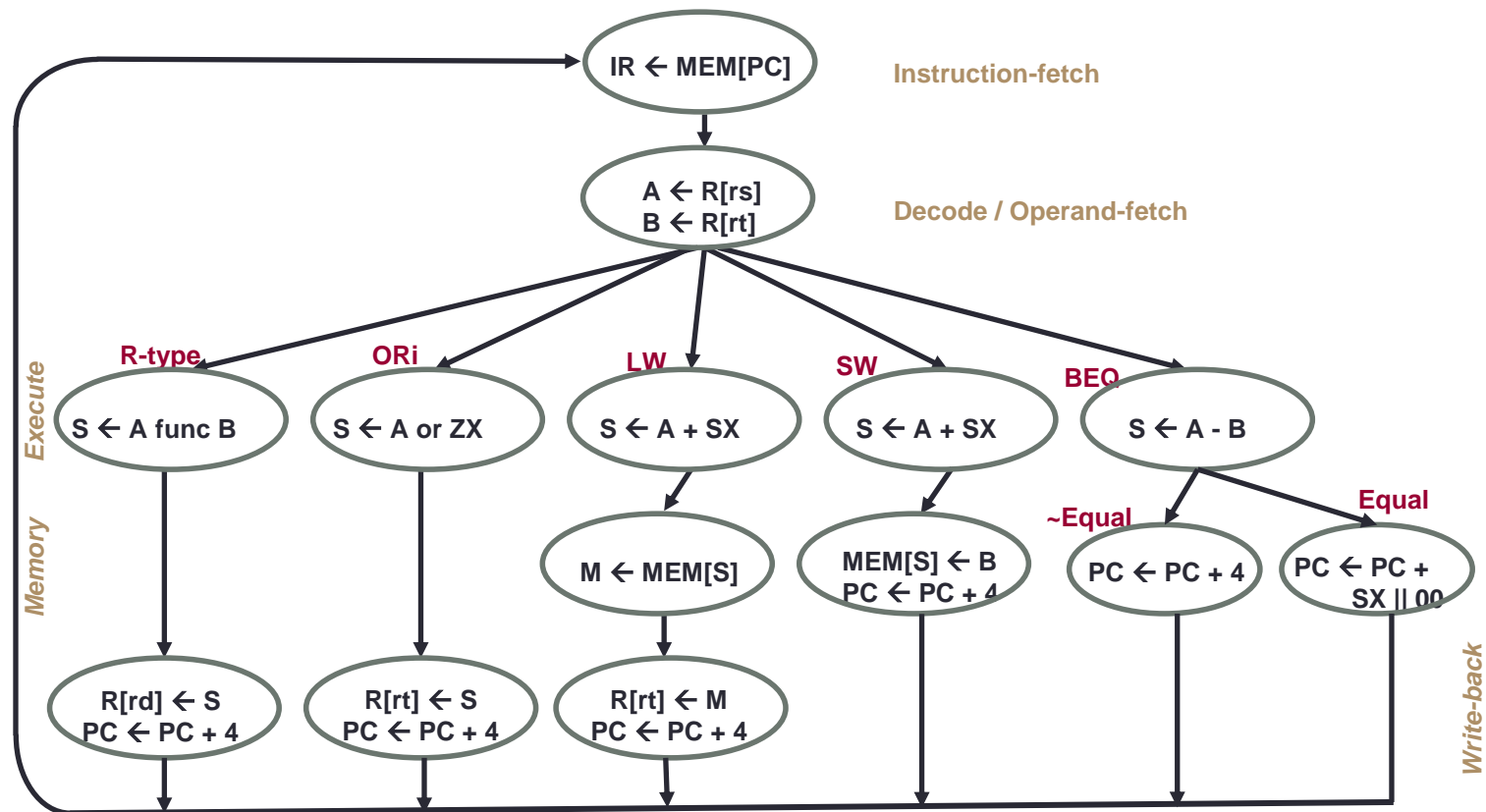- To encode the states of the FSM we just discussed, as shown below, how many bits do we need?




In-class exercise (4)

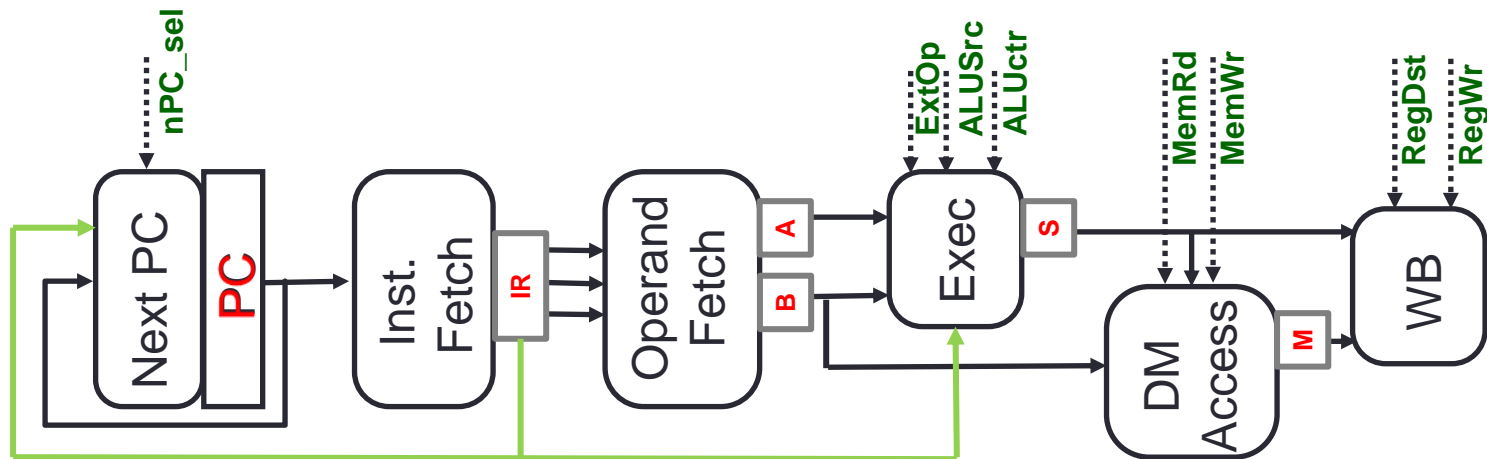- For the BEQ instruction, what control signals are involved?
- What logic expression needs to be implemented for control signal *nPC_sel*?



In-class exercise (5)

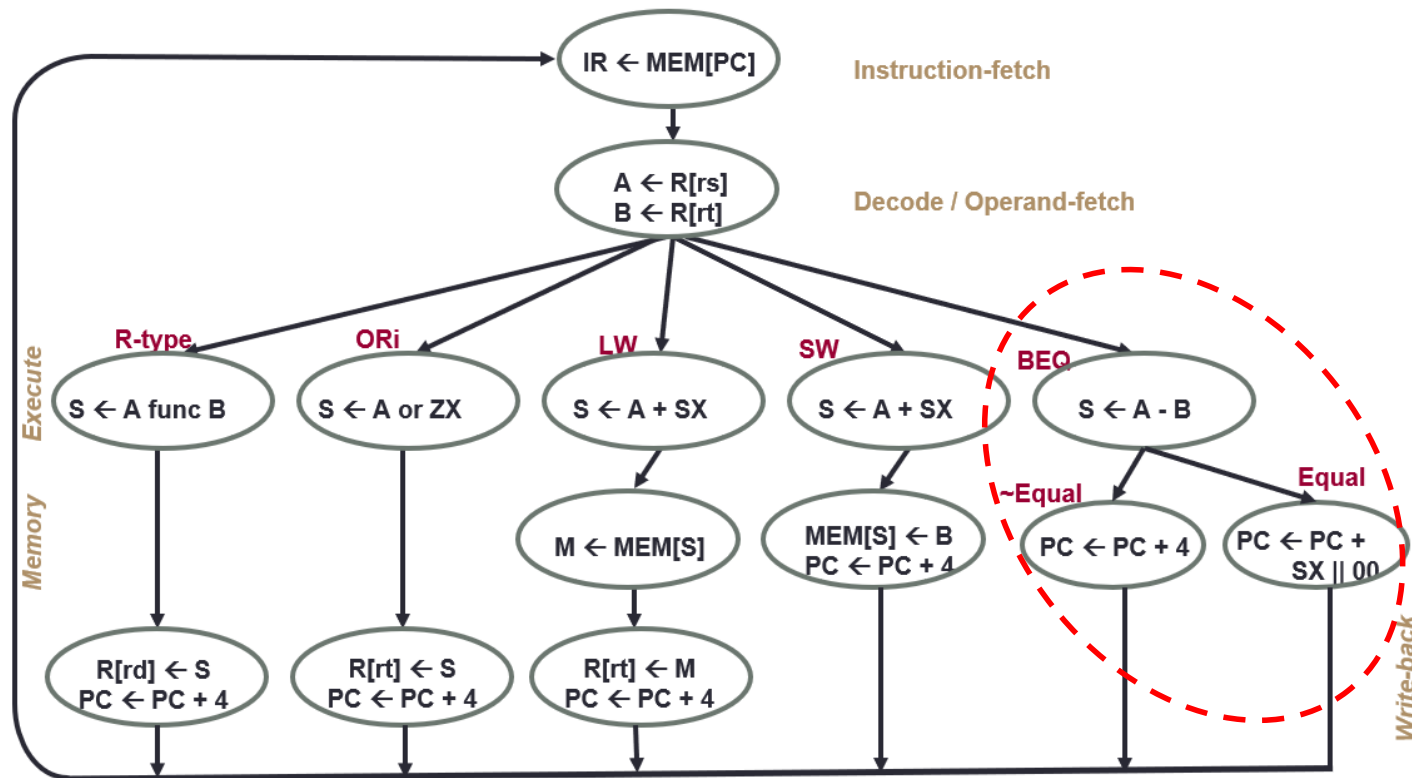- If we merge the three states for BEQ and encode the new state as $G3G2G1G0 = 1111$, what is the new logic expression for nPC_sel ?



In-class exercise (6)

To execute the following code how many clock cycles are needed?

lw	\$10, 20(\$1)
subu	\$11, \$2, \$3
ori	\$13, \$6, \$7
addu	\$14, \$8, \$9