

SINGLE CYCLE PROCESSOR

Lecturer: Hui Annie Guo

h.guo@unsw.edu.au

K17-501F

Lecture overview

- **Topics**
 - **Single-cycle processor**
 - **Datapath**
 - **Control**
- **Suggested reading**
 - **H&P Chapter 4.1-4.4**

Typical steps of processor design

- **Assume ISA is given. To build a processor, we basically go through the following steps:**

For datapath

1. **Analyse instruction set to determine datapath requirements**
2. **Select a set of hardware components for the datapath and establish clocking methodology**
3. **Assemble datapath to meet the requirements**

For control


4. **Analyse implementation of each instruction to determine control points**
 5. **Assemble the control logic**
- **A demonstration with MIPS-Lite is given next**

MIPS-Lite (a sub set of MIPS ISA)

• We demonstrate the datapath design for the following instructions


• ADD and SUB

- ADDU rd, rs, rt
- SUBU rd, rs, rt

 


• OR Immediate:

- ORI rt, rs, imm16

 


• LOAD and STORE

- LW rt, rs, imm16
- SW rt, rs, imm16

 

• BRANCH:

- BEG rs, rt, imm16

 

• JUMP

- J imm26
- covered later



Step 1

- **Analyse instruction set to determine datapath requirements**
 - **For each instruction, its requirement can be identified as a set of register transfer operations**
 - **Data transferred from one storage location to another storage location may go through a combinational logic**
 - **Register-level Transfer Language (RTL) is used to describe the instruction execution**
 - **E.g. $\$3 \leftarrow \$1 + \$2$, for ADDU $\$3, \$1, \$2$**
 - Values in register \$1 and \$2 are added and the result is saved in register \$3
 - **Datapath must support each transfer operation**

MIPS-Lite RTL specifications

Step 1

- All instructions start by fetching instruction,

MEM[PC] = $\boxed{\text{op} \mid \text{rs} \mid \text{rt} \mid \text{rd} \mid \text{shamt} \mid \text{funct}}$ or $\boxed{\text{op} \mid \text{rs} \mid \text{rt} \mid \text{Imm16}}$

instructions in one of the two instruction formats

- Then followed by different operations

Instr. Register Transfers

ADDU	$R[\text{rd}] \leftarrow R[\text{rs}] + R[\text{rt}]; \text{PC} \leftarrow \text{PC} + 4;$
SUBU	$R[\text{rd}] \leftarrow R[\text{rs}] - R[\text{rt}]; \text{PC} \leftarrow \text{PC} + 4;$
ORI	$R[\text{rt}] \leftarrow R[\text{rs}] \vee \text{zero_ext}(\text{Imm16}); \text{PC} \leftarrow \text{PC} + 4;$
LW	$R[\text{rt}] \leftarrow \text{MEM}[R[\text{rs}] + \text{sign_ext}(\text{Imm16})]; \text{PC} \leftarrow \text{PC} + 4;$
SW	$\text{MEM}[R[\text{rs}] + \text{sign_ext}(\text{Imm16})] \leftarrow R[\text{rt}]; \text{PC} \leftarrow \text{PC} + 4;$
BEQ	If ($R[\text{rs}] == R[\text{rt}]$) then $\text{PC} \leftarrow \text{PC} + 4 + \text{sign_ext}(\text{Imm16}) \parallel 00$ else $\text{PC} \leftarrow \text{PC} + 4;$

Requirements of the instruction set

Step 1

- **Memory**
 - instruction & data
- **PC**
- **Registers (let's say 32 x 32)**
 - read rs
 - read rt
 - write rt or rd
- **Add/Sub/Or**
 - on registers, or
 - extended immediate
- **Bit extension**
- **Add**
 - $PC + 4$
 - $PC + 4 + \text{extended immediate}$


Step 2:

- **Select a set of components for the datapath and establish clocking methodology**
 - **Combinational elements**
 - **Storage elements**
 - **Clocking methodology**


Step 2

Combinational logic elements


- adder**

 

- MUX**

 

- ALU**

 


- Other components**

- Added as we go

Step 2

Storage elements: registers

 - **A register consists of a set of Flip Flops**
 - **32-bit input and output**
 - **Write Enable input**
 - **0: disable**
 - **1: enable**




Storage elements: register file

Step 2

- **Register File (RF) consists of 32 registers:**

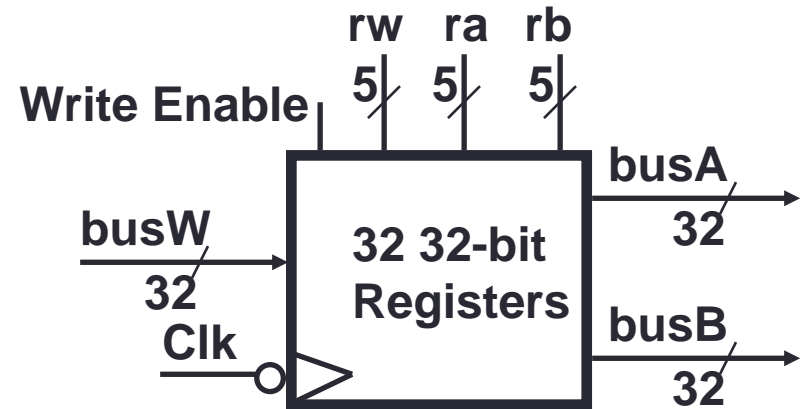- **Two 32-bit output ports/buses:**
 - **busA and busB**
- **One 32-bit input port/bus: busW**



- **Register is selected by ra, rb, rw:**

- $(ra) \rightarrow \text{busA}$
- $(rb) \rightarrow \text{busB}$
- $(rw) \leftarrow \text{busW}$ if Write Enable is 1

- **Clock input (Clk)**


- The Clk input is often used for write operation

Note: (*) represents the content of a storage location.

Storage elements: memory

Step 2

 - **Memory (idealized)**
 - One input port/bus: Data In
 - One output port/bus: Data Out




- **Memory word is selected by Address**
 - (Address) \rightarrow Data Out
 - (Address) \leftarrow Data In if Write Enable = 1
- **Clock input (Clk)**
 - The Clk input is used for write operation

Typical clocking methodology

Step 2

 - **Edge triggered clocking**
 - All storage elements are clocked by the same clock edge.
 - Simple and robust
- **Issues need to be considered**
 - **Clock skew**
 - difference in clock arrival time at different storage components
 - **Setup time**
 - Period of stable input for the register to read
 - **Hold time**
 - Period of stable input for the register output




Typical clocking methodology (cont.)

Step 2

- Two requirements for saving a new data into a register:

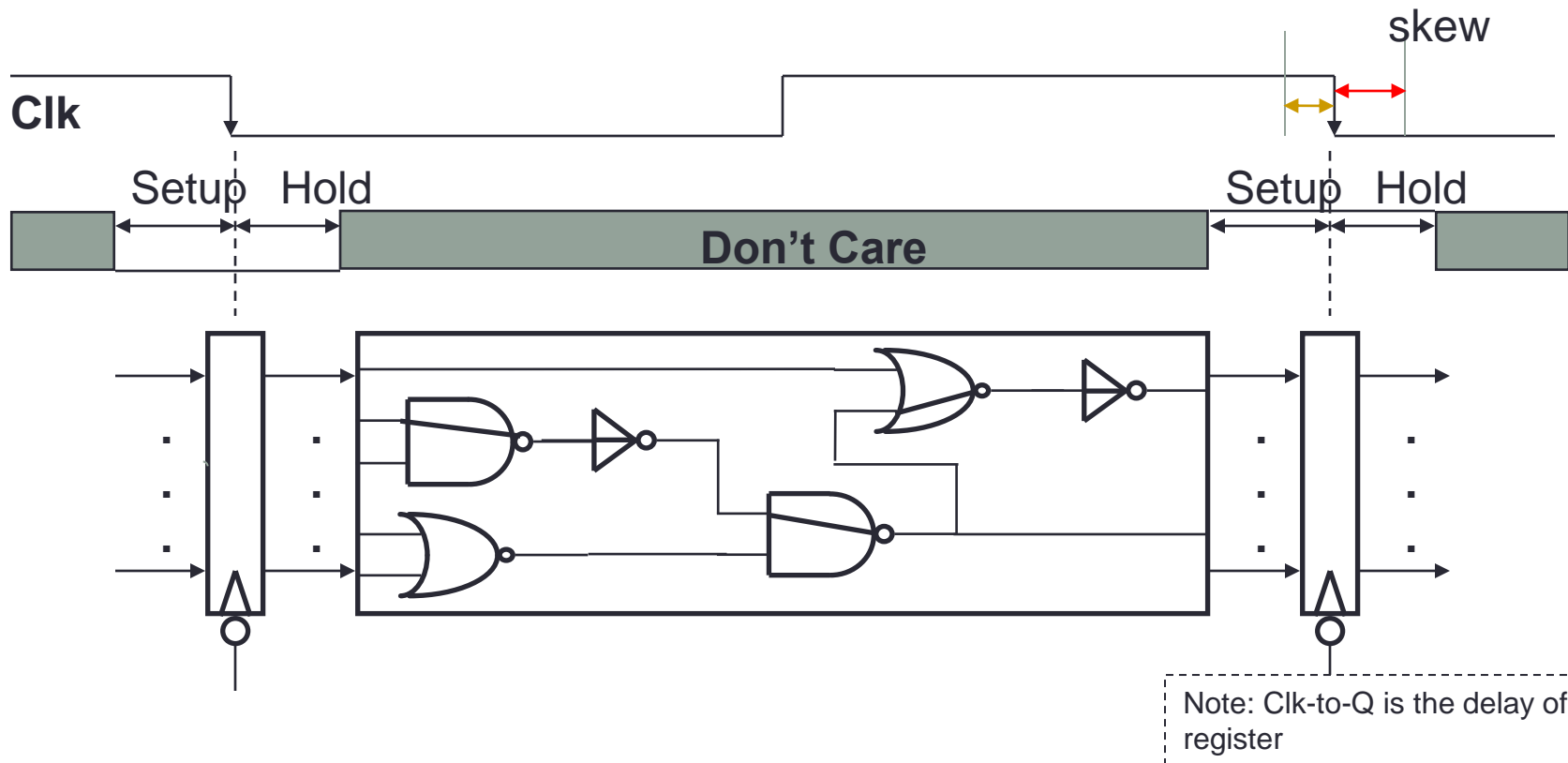- $\text{Cycle Time} \geq \text{Clk-to-Q} + \text{Longest Delay Path} + \text{Setup} + \text{Clock Skew}$
- $(\text{Clk-to-Q} + \text{Shortest Delay Path} - \text{Clock Skew}) > \text{Hold Time}$




Step 3

- **Assemble datapath to meet the requirements**
 - Put the selected components together based on the register transfer requirements
 - It can start with each step of the instruction execution cycle
 - Instruction Fetch
 - Read Operands
 - Execute Operation
 - Next Instruction
 - See next a few slides for details

For all instructions

Step 3

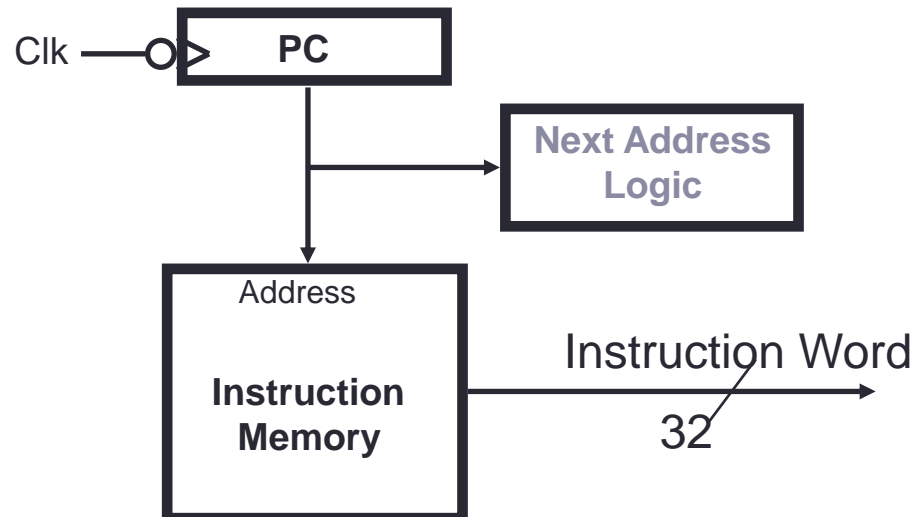- **Instruction fetch unit:**
 - **At the start of clock cycle, fetch instruction:**
MEM[PC]
 - **At the end of the cycle, update the program counter:**
 - **For sequential code execution:** $PC \leftarrow PC + 4$
 - **For branch:** $PC \leftarrow \text{"something else"}$
 - Will be covered later




For *ADDU* and *SUBU*

Step 3

$R[rd] \leftarrow R[rs] \text{ op } R[rt]$

e.g. *ADDU rd, rs, rt*

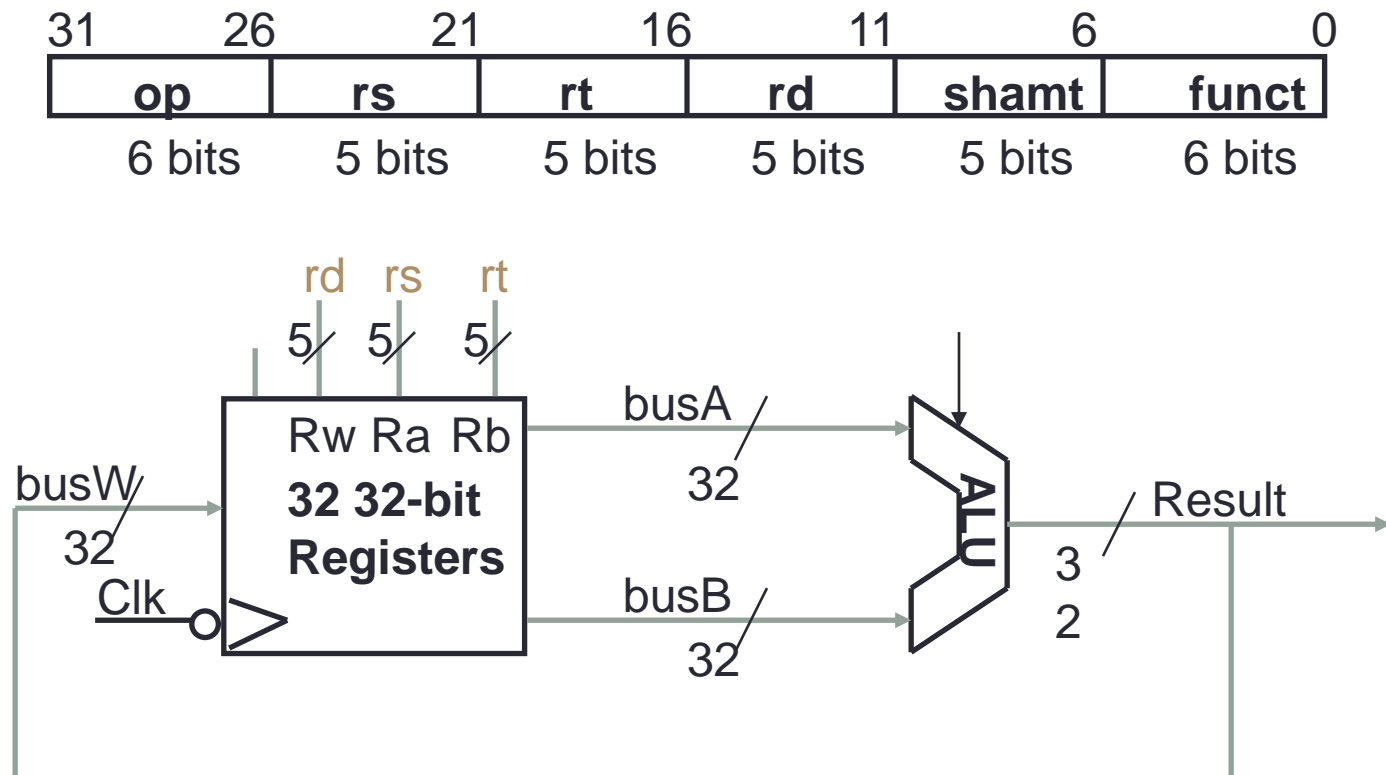- **Ra, Rb, and Rw** come from instruction's **rs, rt, and rd** fields




For *ORi*

Step 3

$R[rt] \leftarrow R[rs] \text{ op ZeroExt}[imm16]$


e.g. *ORi* *rt*, *rs*, *imm16*

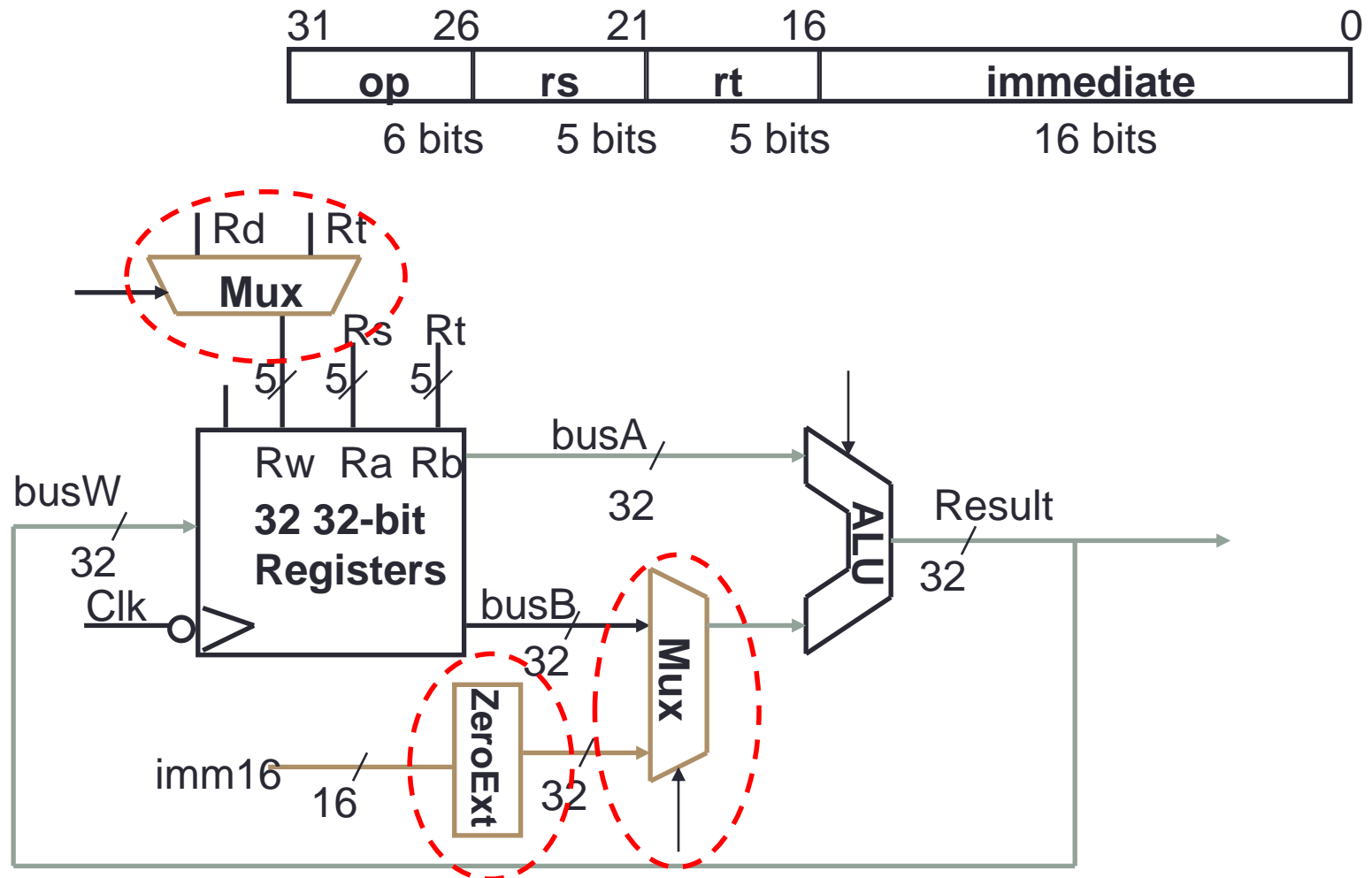

For *LW*

Step 3


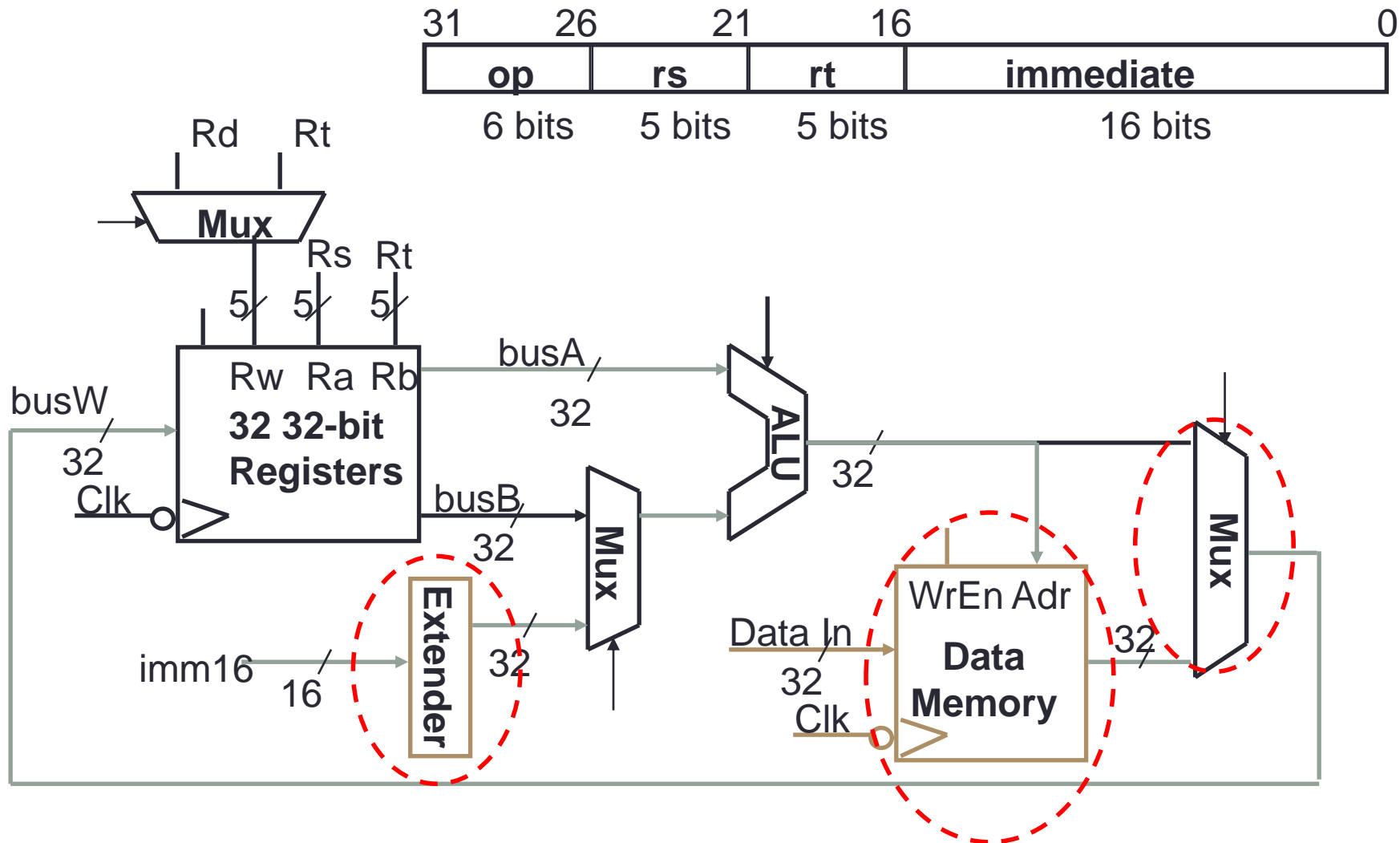
$R[rt] \leftarrow MEM[R[rs] + SignExt[imm16]]$ e.g. *LW rt, rs, imm16*



For SW

Step 3

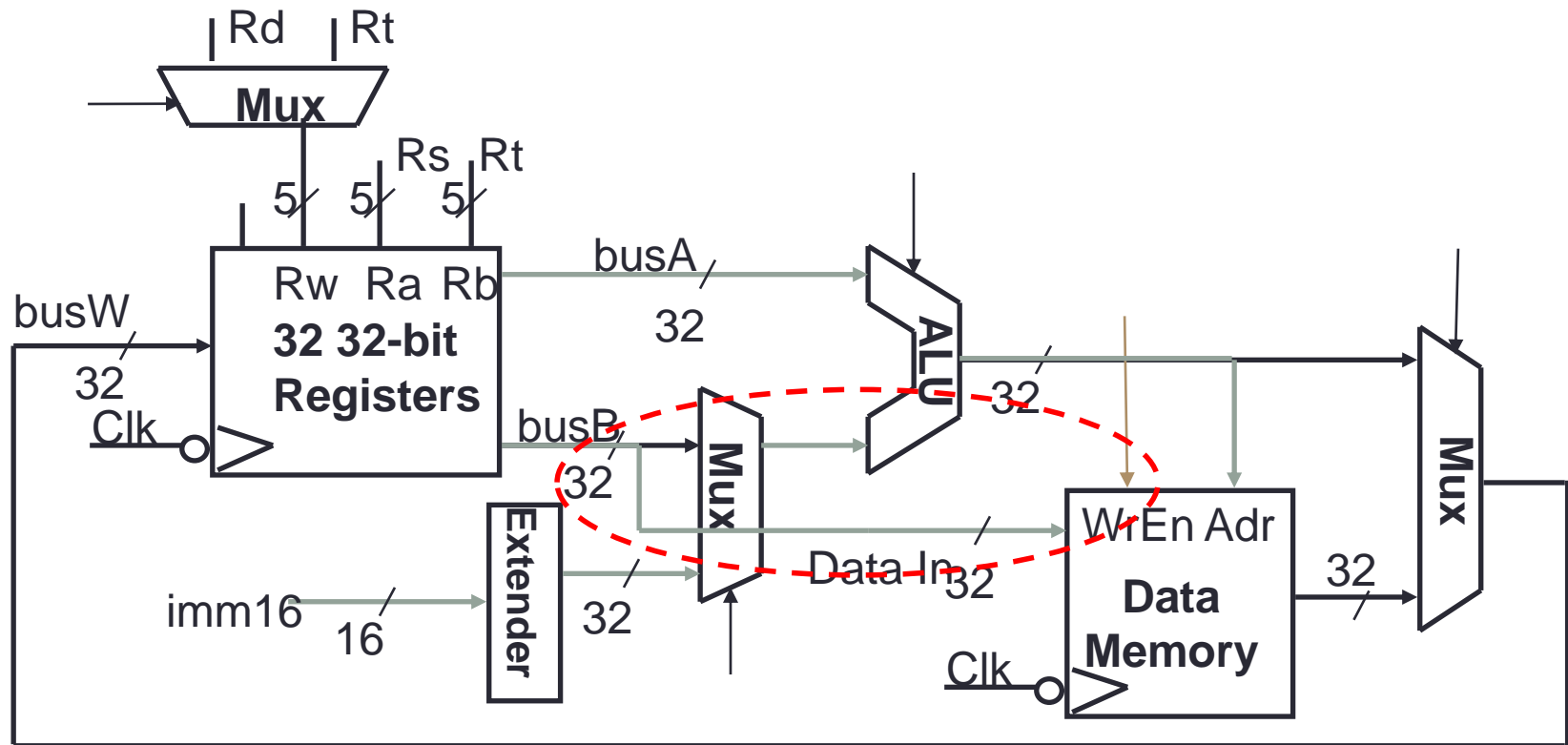 
$MEM[R[rs] + SignExt[imm16]] \leftarrow R[rt]$ e.g. SW $rt,rs,imm16$




For *BEG*

Step 3

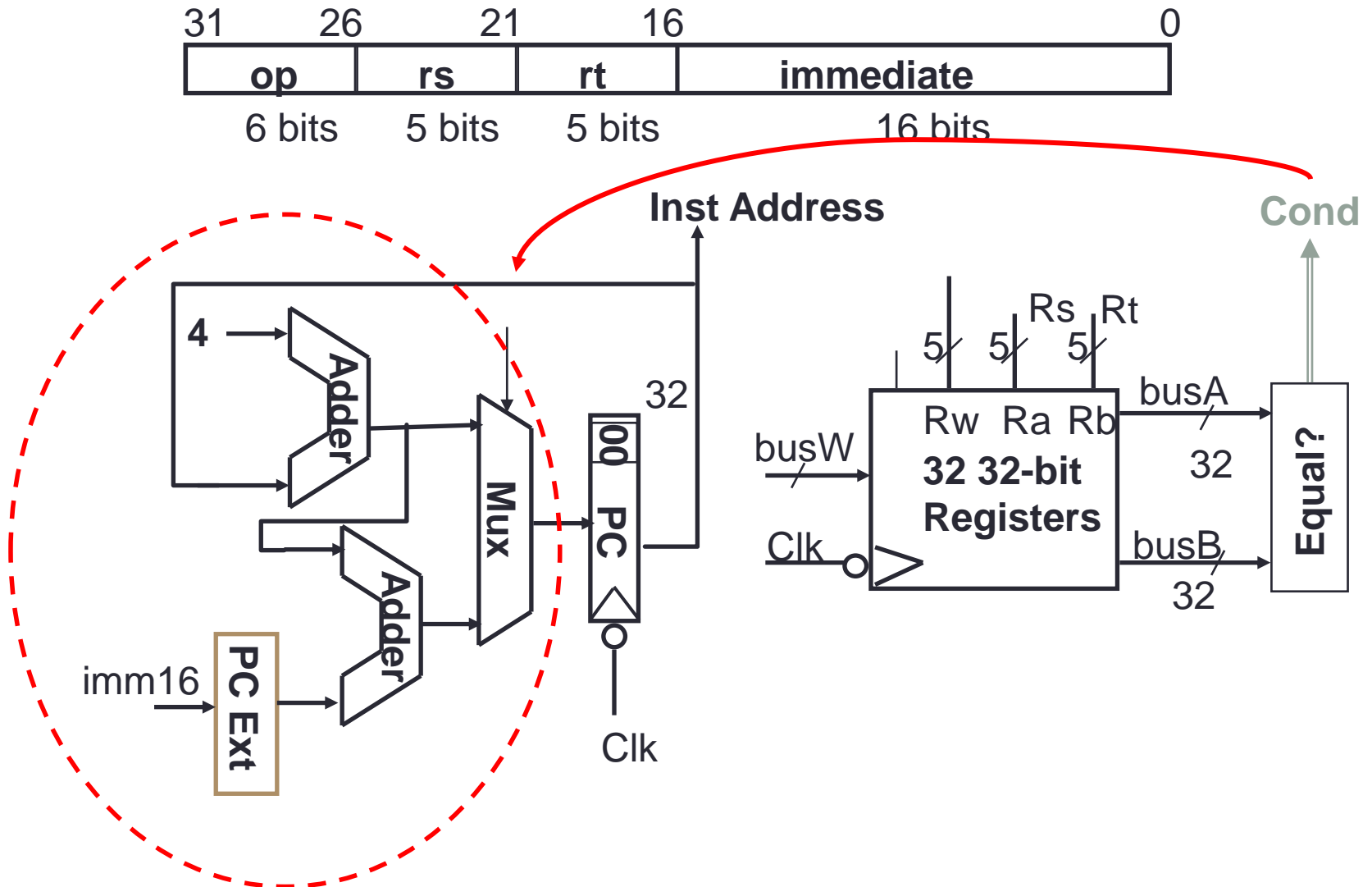BEG *rs, rt, imm16* (Datapath generates the condition, equal)



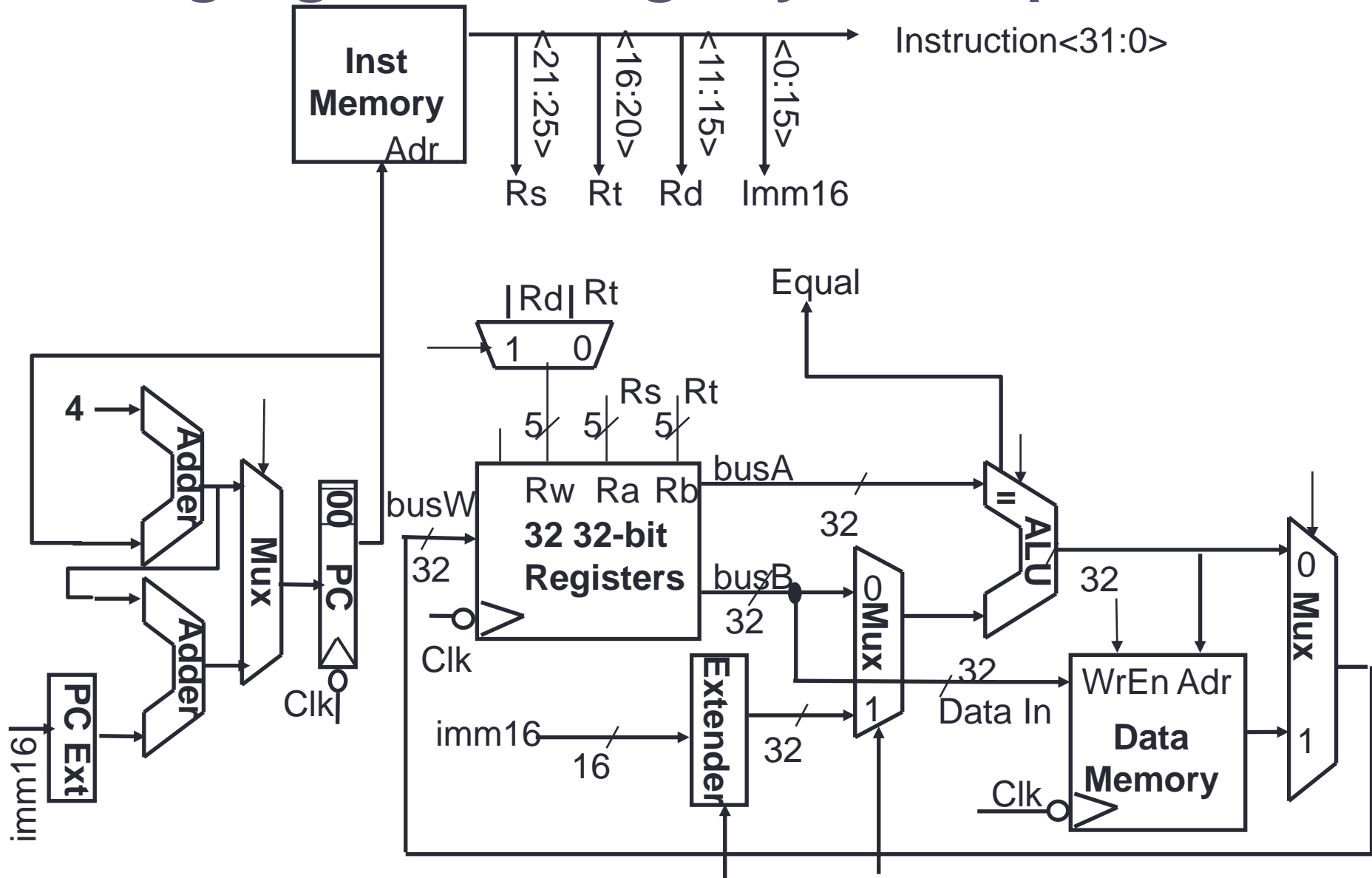Putting together: a single cycle datapath



Instruction encoding

- **Instruction encoding uses binary code to represent operations and operands.**
 - See MIPS [reference data sheet](#) in the textbook for MIPS instruction encoding
 - Example

Instr.	R-type	ori	lw	sw	beq	jump
op	000000	001101	100011	101011	000100	000010

R-type Instr.	add	sub	and	or
funct	100000	100010	100100	100101

- **Control unit design is closely related to instruction encoding**
 - Here we only discuss how to design the control unit given the MIPS encoding

Recall: Typical steps of processor design (this lecture)

- **Assume ISA is given. To build a processor, we basically go through the following steps:**

For datapath

1. **Analyse instruction set to determine datapath requirements**
2. **Select a set of components for the datapath and establish clocking methodology**
3. **Assemble datapath to meet the requirements**

For control

4. **Analyse implementation of each instruction to determine control points**
5. **Assemble the control logic**


- **A demonstration is given below.**

Step 4


- **Analyse implementation of each instruction to determine control points**
 - **Here we consider single cycle datapath**
 - **Control needs to make sure each instruction to be completed in one clock cycle**

Control points

Step 4

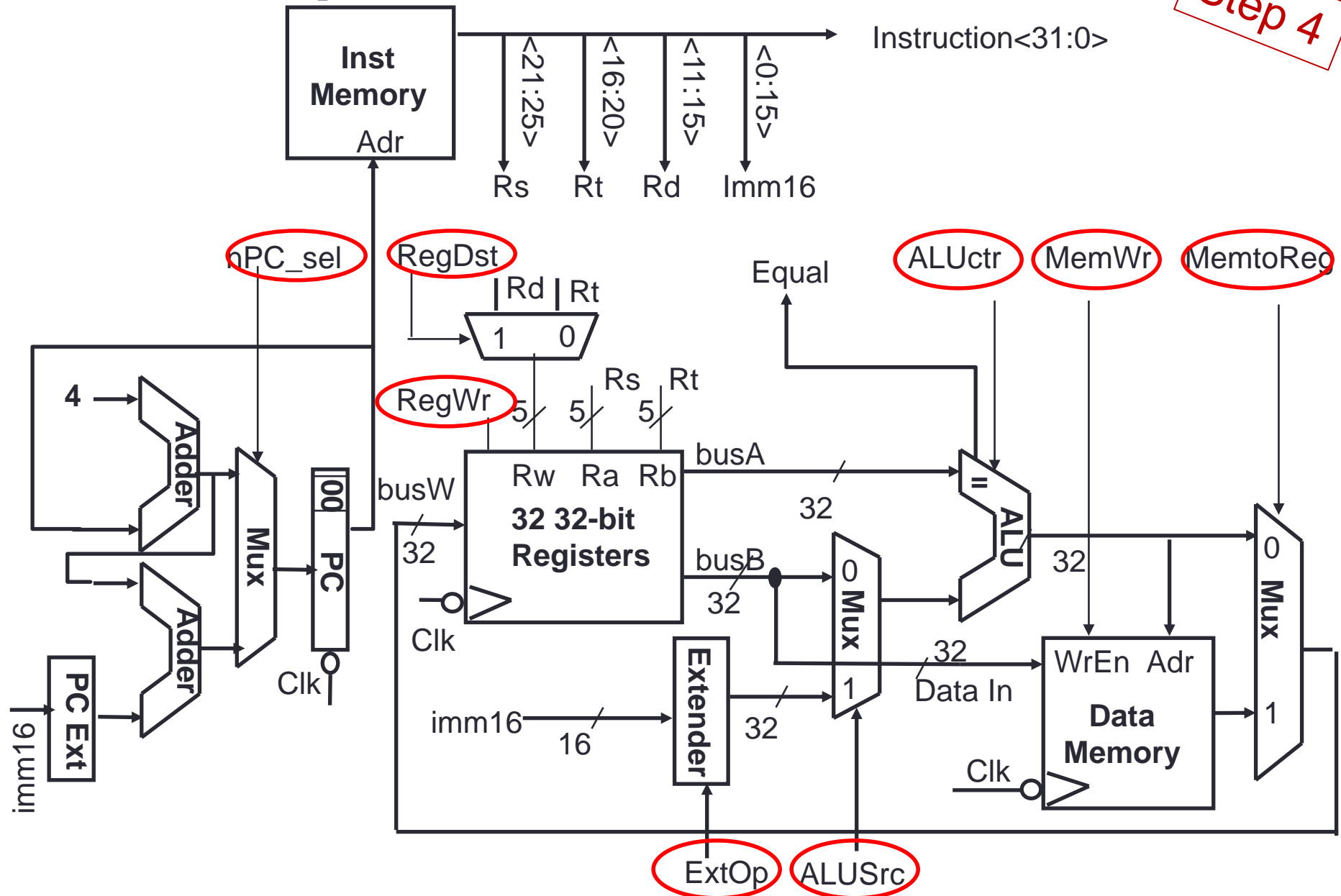


What do we need to do next?

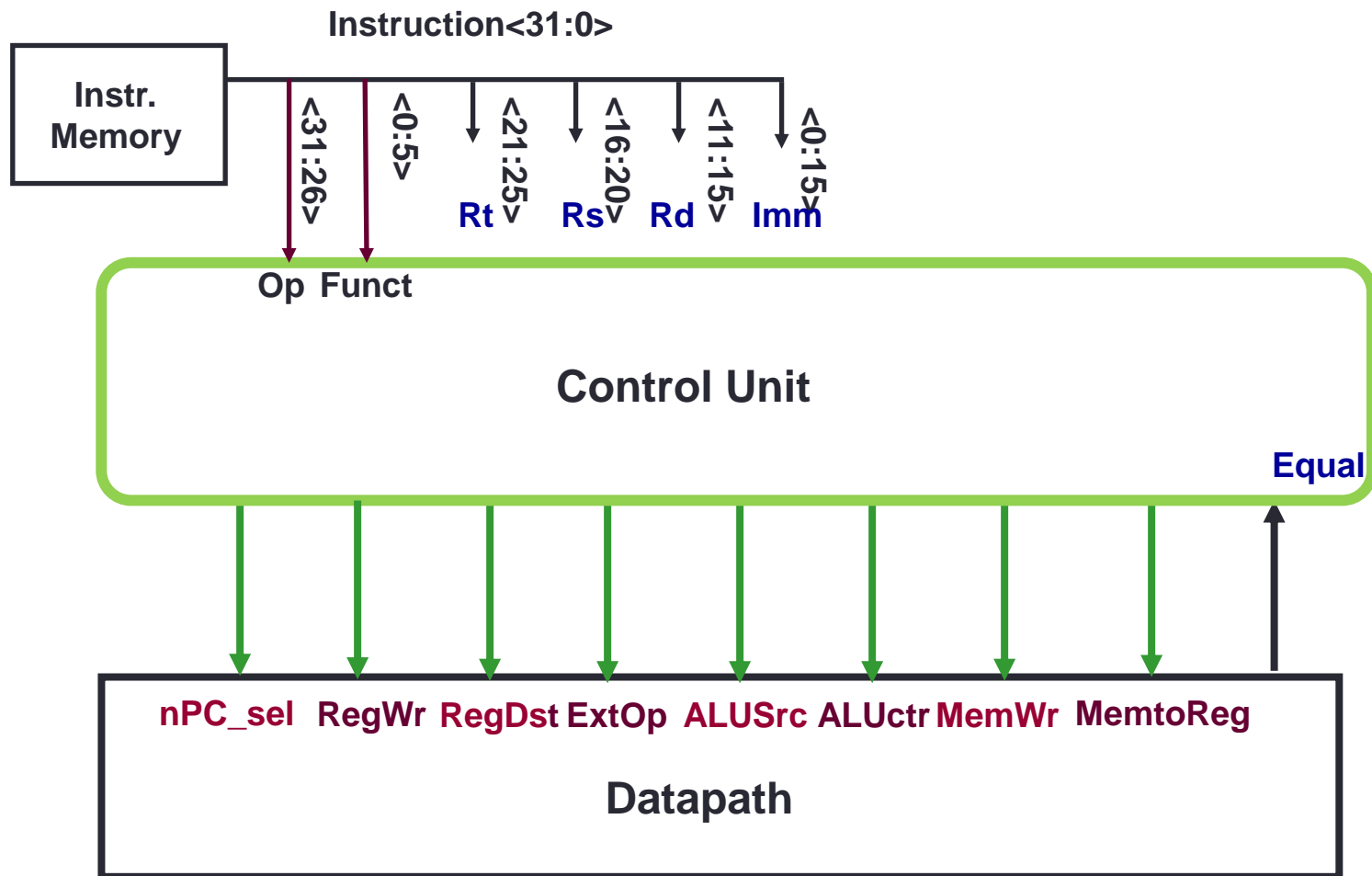

Step 5

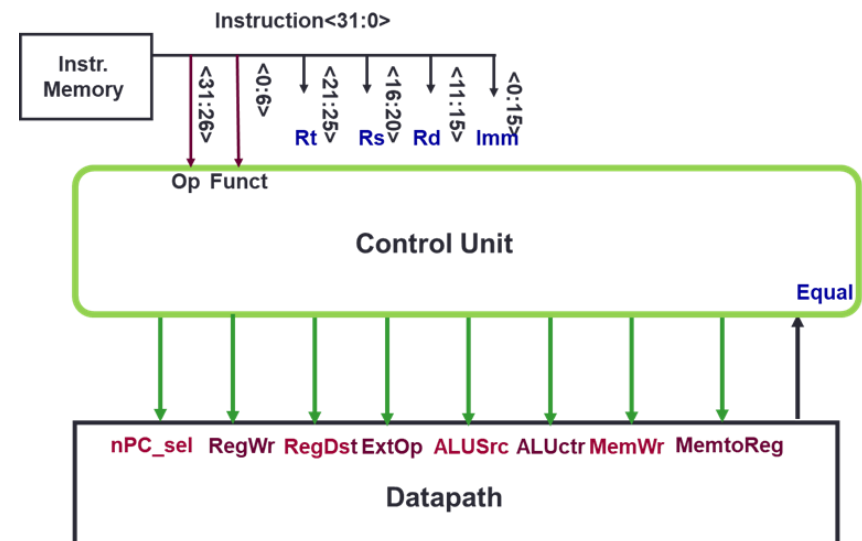- **Assemble control logic**
 - Determine the logic function of each control signal
 - Design to implement those functions
- **The logic can be very large**
 - Should be carefully designed



Logic for each control signal


Step 5

nPC_sel:	if (OP == BEQ) then Equal else 0
ALUsrc:	if ((OP == "000000") (OP == BEQ)) then "regB" else "Imm"
ALUctr:	if (OP == "000000") then Funct elseif (OP == ORi) then "or" elseif (OP == BEQ) then "sub" else "add"
ExtOp:	if (OP == ORi) then "zero" else "sign"
MemWr:	if (OP == SW)
MemtoReg:	if (OP == LW)
RegWr:	if ((OP == SW) (OP == BEQ)) then 0 else 1
RegDst:	if ((OP == LW) (OP == ORi)) then 0 else 1

Step 5

Control logic with two levels

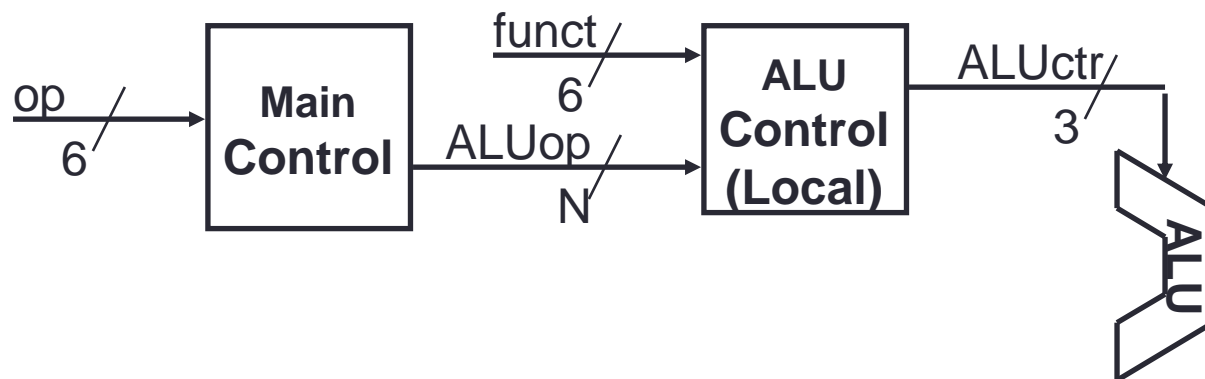- A single level of control logic may be costly
- Local decoding for ALU operations makes design simpler, smaller and faster.




Truth table for main control

Step 5


op	000000	001101	100011	101011	000100	000010
	R-type	ori	lw	sw	beq	jump
RegDst	1	0	0	x	x	x
ALUSrc	0	1	1	1	0	x
MemtoReg	0	0	1	x	x	x
RegWrite	1	1	1	0	0	0
MemWrite	0	0	0	1	0	0
Branch	0	0	0	0	1	0
Jump	0	0	0	0	0	1
ExtOp	x	0	1	1	x	x
ALUOp(Symbolic)	"R-type"	Or	Add	Add	Subtract	xxx
ALUOp <2>	1	0	0	0	0	x
ALUOp <1>	0	1	0	0	0	x
ALUOp <0>	0	0	0	0	1	x

PLA implementation of the main control


Step 5

 

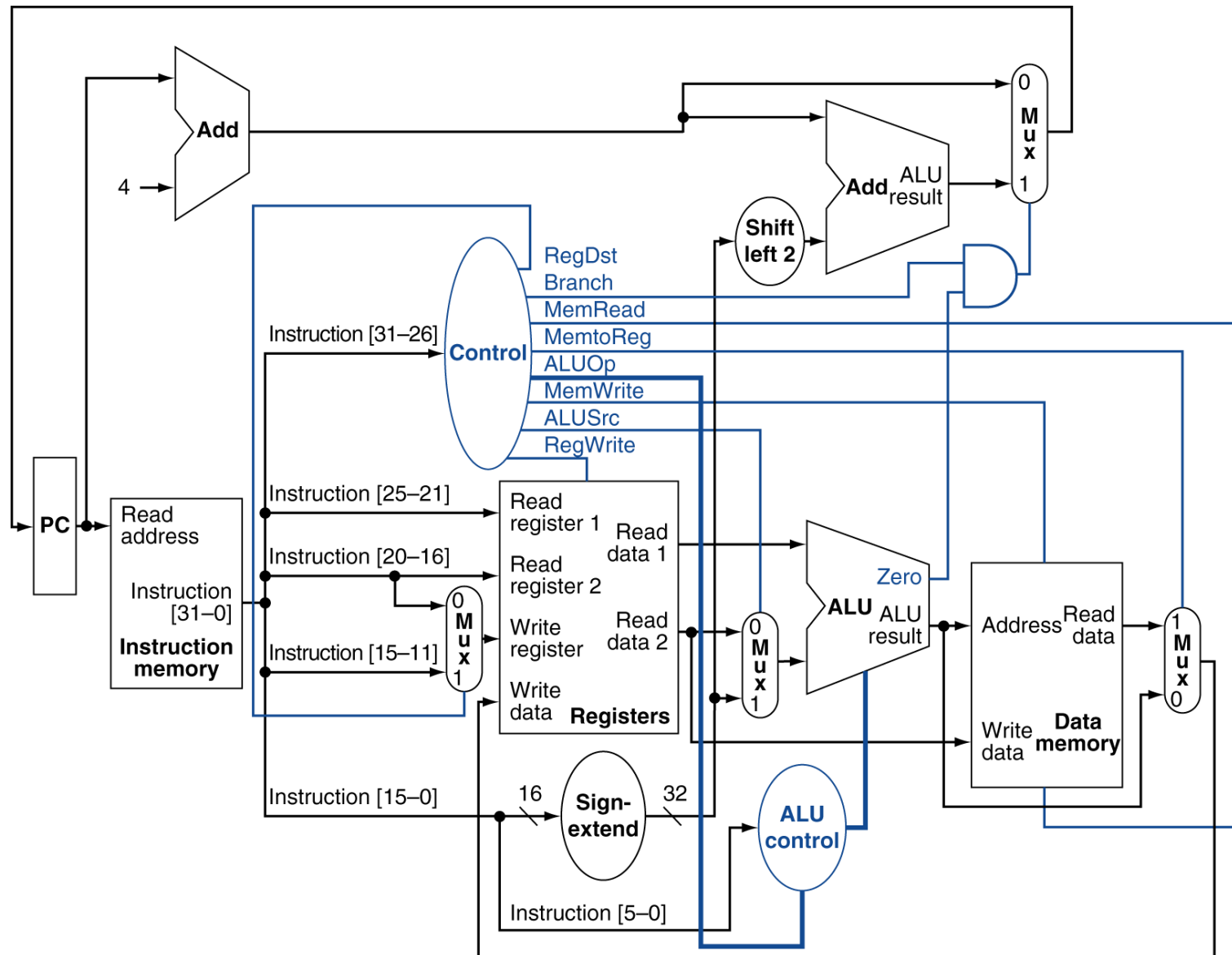
Putting it all together: a single cycle processor



Single Cycle Processor with Jump Added

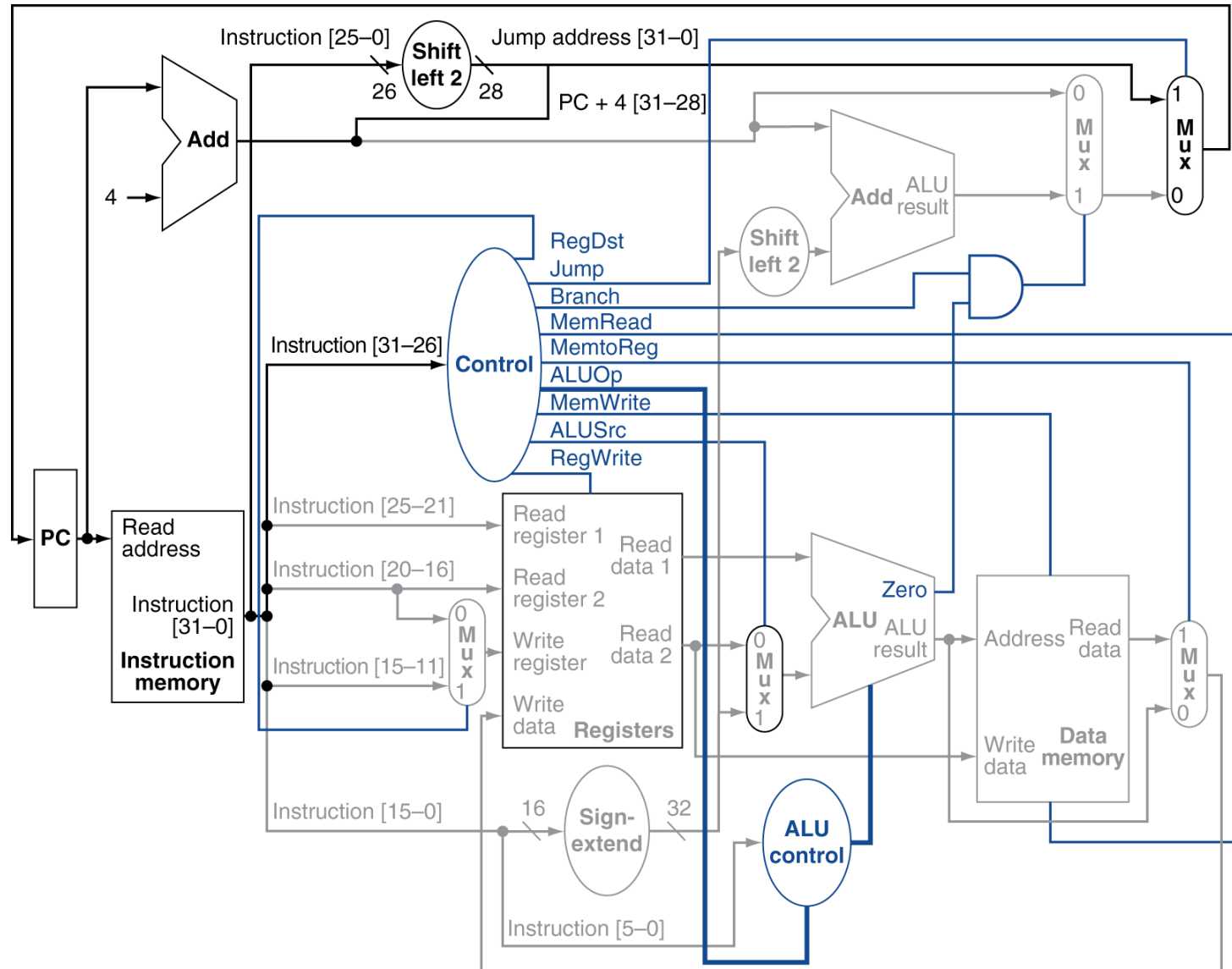

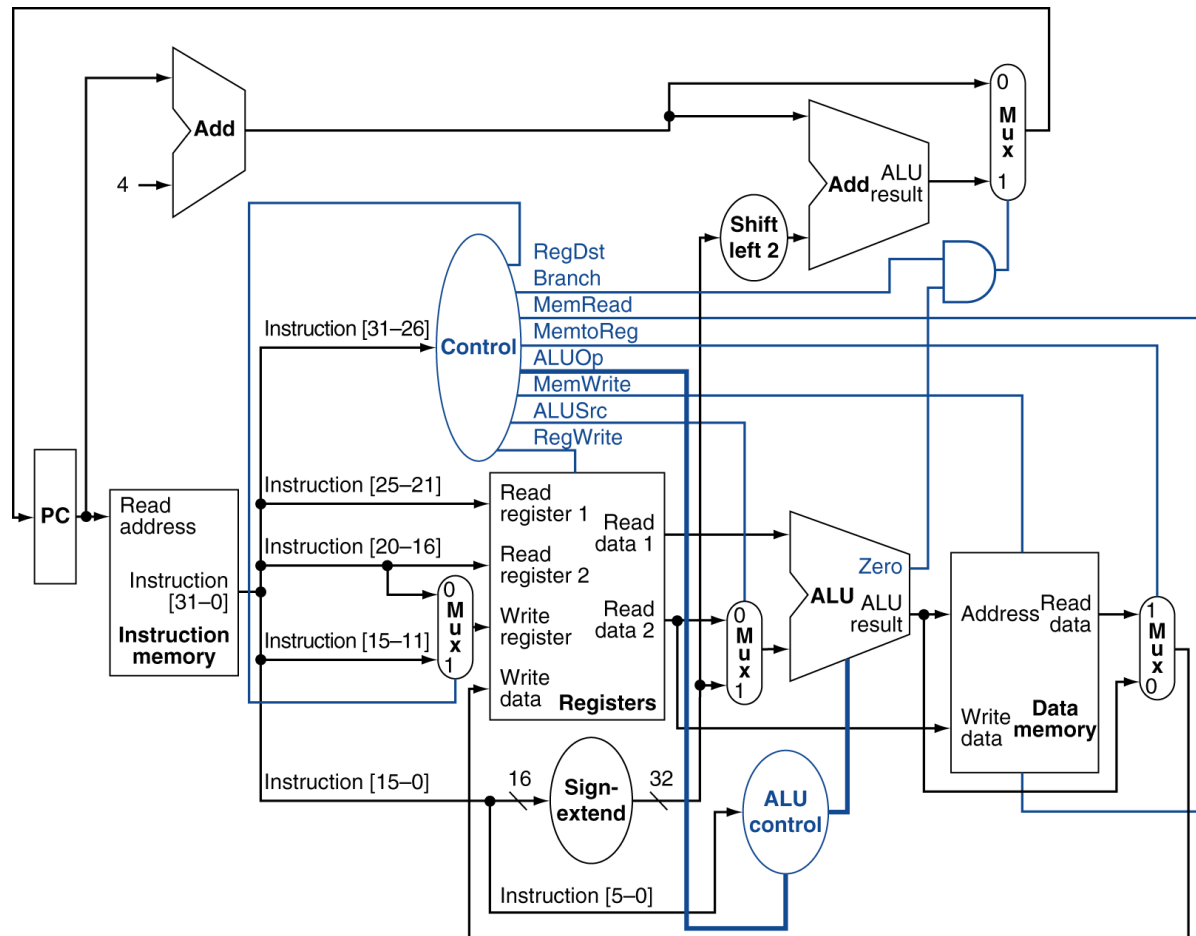- **Given the processor design below, identify the datapath components for R-type instructions and BEQ instruction.**



In-class exercise 2

- **Can we use the MIPS-Lite processor we just built to solve the following problem? Why? Assume x and y are unsigned integers and can be stored in registers.**

```
if (x > y)
    y++
else
    y--
```